

IN ORDER TO COMPLETE OBJECTIVE 4:


In the two diagrams, trace the path of the current through the circuit when the switches indicated by arrows are pressed.

Start at the positive end of the batteries and use a RED marker to trace the path to the motor.

Then use a BLACK marker to trace the path back to the negative end of the batteries.

Don't forget to go online and answer the questions!

PRESS SWITCHES A7 & B7:

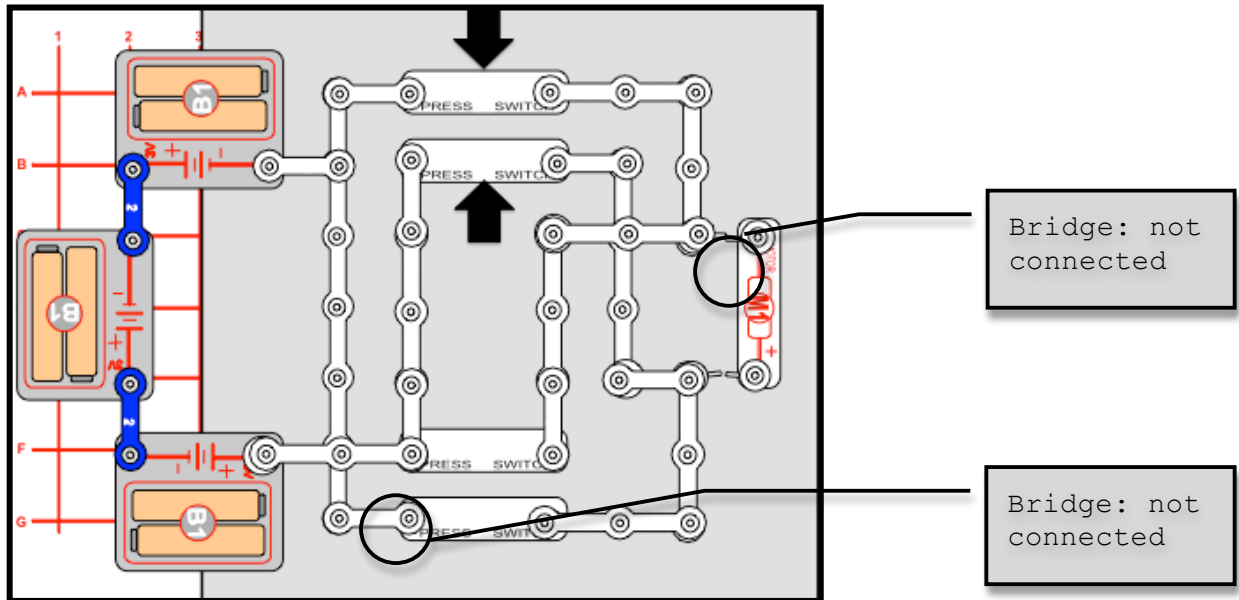

PRESS SWITCHES F7 & G7:

